
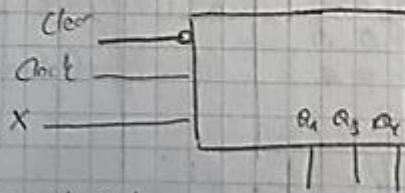


Multi Mode Counter

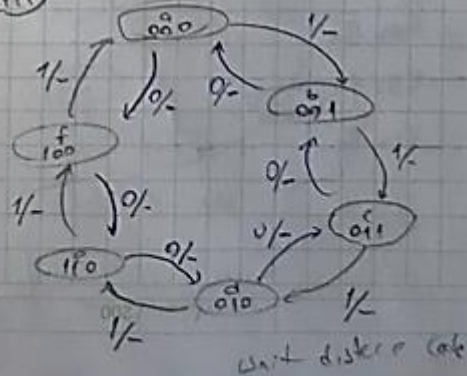- Three bits
- Unit Dist. Code
- Mod 6
- Sync
- Up/Down



(101) ϕ



Format X/-

X=1 0 k/gunde
X=0 0 k.

Veriye de
giriş de

24

050W

	A _n	B _n	C _n	X	A _{n+1}	B _{n+1}	C _{n+1}	J _n	K _n	J _{n+1}	K _{n+1}	J _{n+2}	K _{n+2}
0	0	0	0	0	1	0	0	1	0	0	0	0	0
1	0	0	0	1	0	0	1	0	0	0	0	0	0
2	0	0	1	0	0	0	0	0	0	0	0	0	1
3	0	0	1	1	0	1	1	0	0	1	0	0	0
4	0	1	0	0	0	1	1	0	0	0	0	1	0
5	0	1	0	1	1	1	0	1	0	0	0	0	0
6	0	1	1	0	0	0	1	0	0	0	1	0	0
7	0	1	1	1	0	1	0	0	0	0	0	0	1
8	1	0	0	0	1	1	0	0	0	1	0	0	0
9	1	0	0	1	0	0	0	0	1	0	0	0	0
10	1	0	1	0	0	0	0	0	0	0	0	0	0
11	1	0	1	1	0	0	0	0	0	0	0	0	0
12	1	1	0	0	0	1	0	0	1	0	0	0	0
13	1	1	0	1	1	0	0	0	0	0	1	0	0
14	1	1	1	0	0	0	0	0	0	0	0	0	0
15	1	1	1	1	0	0	0	0	0	0	0	0	0

K_{MAX}

$$Q_A = \bar{C}_n (B_n \oplus X)$$

$$Q_B = A_n \bar{X} + \bar{A}_n B_n \bar{C}_n + C_n X$$

$$Q_C = \bar{A}_n (B_n \oplus X)$$

$$J_A = \bar{C}_n (B_n \oplus X)$$

$$K_A = B_n \oplus X$$

$$J_B = A_n \bar{X} + C_n X$$

$$K_B = A_n \bar{X} + C_n X$$

$$K_C = A_n X + C_n \bar{X}$$

$$J_C = \bar{A}_n (B_n \oplus X)$$

$$K_C = B_n \oplus X$$

RING COUNTERS (Johnson or Möbius counter)

1) Standard-Ring code \rightarrow Counter

2) Twisted-Ring code \rightarrow Counter

Standard Ring code
(one-hot counter)

A B C D	A B C D
0 0 0 0	0 0 0 0
1 0 0 0	0 0 0 1
0 1 0 0	0 0 1 0
0 0 1 0	0 1 0 0
0 0 0 1	1 0 0 0
0 0 0 0	0 0 0 0



4. sırada sadece MSB veya LSB
hissi vardır diğer bitler aynıdır.

Twisted-Ring code
(Johnson counter, Möbius counter)

A B C	A B C
0 0 0	0 0 0
1 0 0	0 0 1
1 1 0	0 1 1
1 1 1	1 1 1
0 1 1	1 1 0
0 0 1	1 0 0
0 0 0	0 0 0

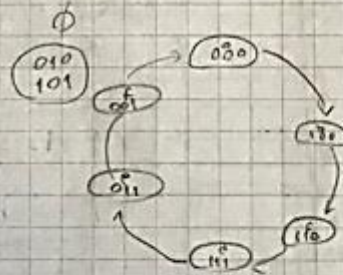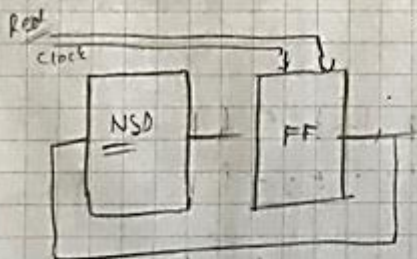4. sırada ise MSB veya LSB'de
başlangıç her seferinde
bir sonraki bitin olduğu
yerde olur diğer bitler aynı
olarak önceki bitleri takip eder.

3 bit twisted ring counter
tasarım (MSB evirildi olsun)




A _n	B _n	C _n	D _n	D _{n+1}	C _{n+1}	B _{n+1}	A _{n+1}	J _A	K _A	J _B	K _B	J _C	K _C
0	a	0	0	0	1	0	0	1	0	0	0	0	0
1	f	0	0	1	0	0	0	0	0	0	0	0	1
2	0	0	1	0	0	0	0	0	0	0	0	0	0
3	e	0	1	1	0	0	1	0	0	0	1	0	0
4	b	1	0	0	1	1	0	0	0	0	1	0	0
5	0	1	0	1	0	0	0	0	0	0	0	0	0
6	c	1	1	0	1	1	1	0	0	0	0	1	0
7	d	1	1	1	0	1	1	0	1	0	0	0	0

NSD for D FF


NSD for JK FF

OSOW

$$\begin{array}{l|l} D_A = \bar{C} & J_A = \bar{C} \\ D_B = A & J_B = A \\ D_C = B & J_C = B \end{array} \quad \begin{array}{l} K_A = C \\ K_B = \bar{A} \\ K_C = \bar{B} \end{array}$$

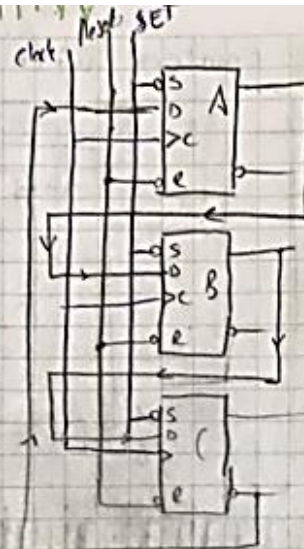

RIPPLE (ASYNCHRONOUS) COUNTERS

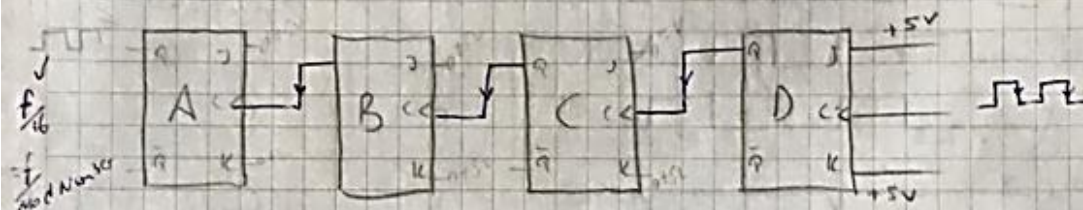


$\frac{f}{2^N}$

MOD NUMBER = 2^N

$n=4 \quad 2^N = 16 \rightarrow \text{Mod } 16$

clock ripple

	A	B	C	D
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

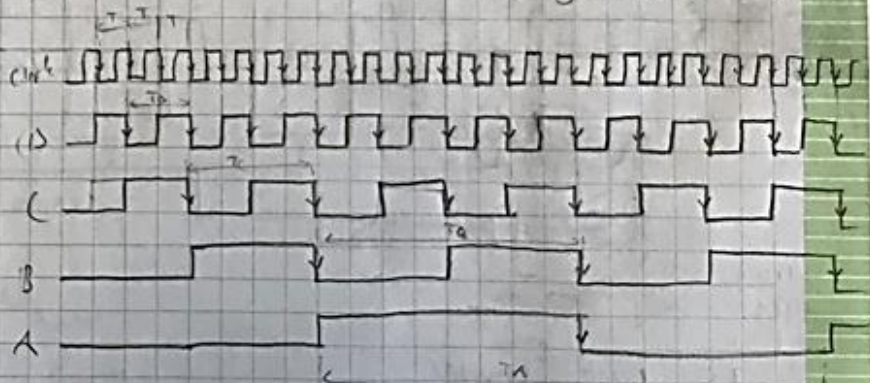

$$f_C = \frac{f_0}{2} = \frac{f}{4}$$

$$f_B = \frac{f_C}{2} = \frac{f}{8}$$

$$f_A = \frac{f_B}{2} = \frac{f}{16} = \frac{f}{\text{Mod Number}} = \frac{f}{2^N}$$

$$T_{\text{out}} = 2T$$


$$\frac{1}{f} = 2 \cdot \frac{1}{f}$$

$$f_0 = \frac{f}{2}$$


OSOW

counters with Mod Number $< 2^N$

	A	B	C
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
	1	1	0

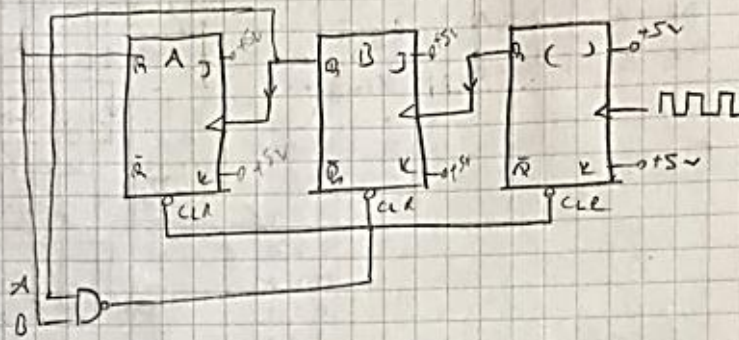


MOD 6

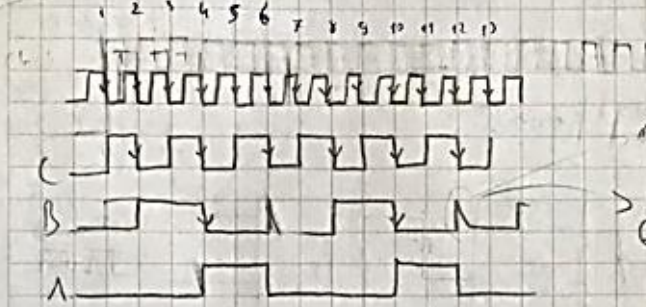

NAND Output

Mod 14 ripple counter design

MOD 14

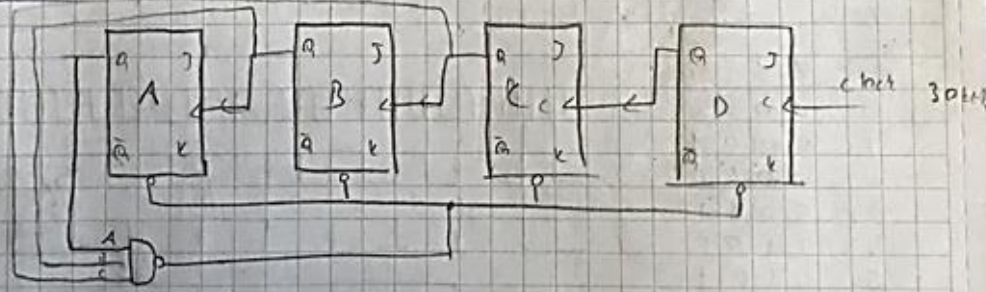



1101 -> 13
1110 -> 14

JC Ripple Counter


TTL (7493, 74293)

CMOS: 74HC 2024, 74HC 4040
(7617) (12617)


OSOW

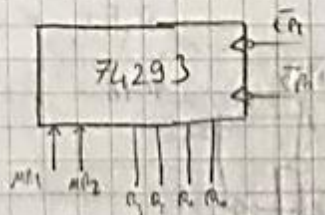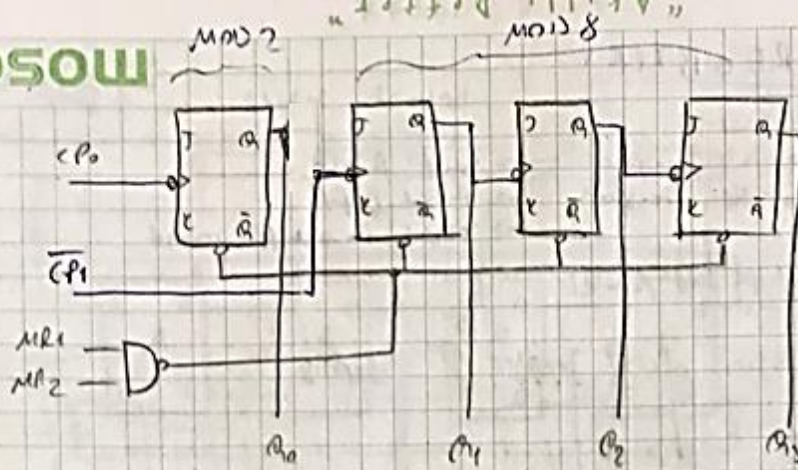

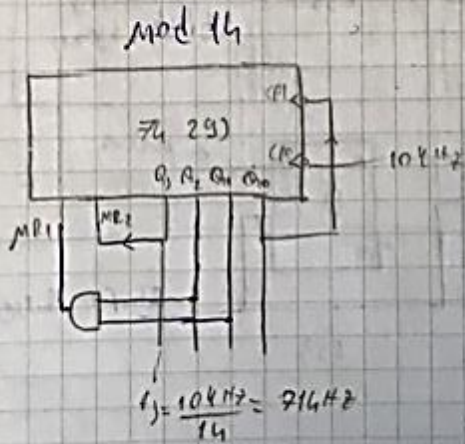
$$f_3 = \frac{f}{16} = \frac{10 \text{ kHz}}{16} = 625 \text{ Hz}$$


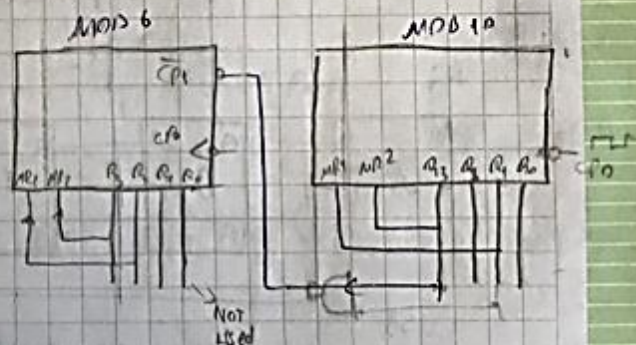
$$f_3 = \frac{10 \text{ kHz}}{14} = 714 \text{ Hz}$$



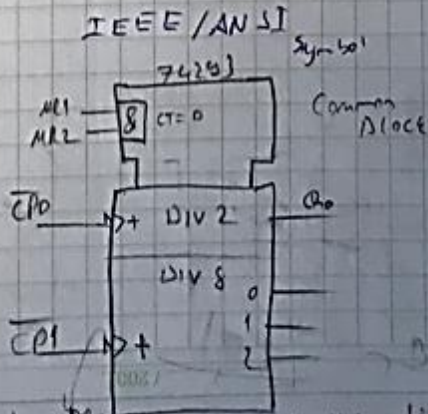
$$\text{MOD } 60 = \text{MOD } 6 \cdot \text{MOD } 10$$








Synchronous counters

A 2-bit synchronous binary counter.

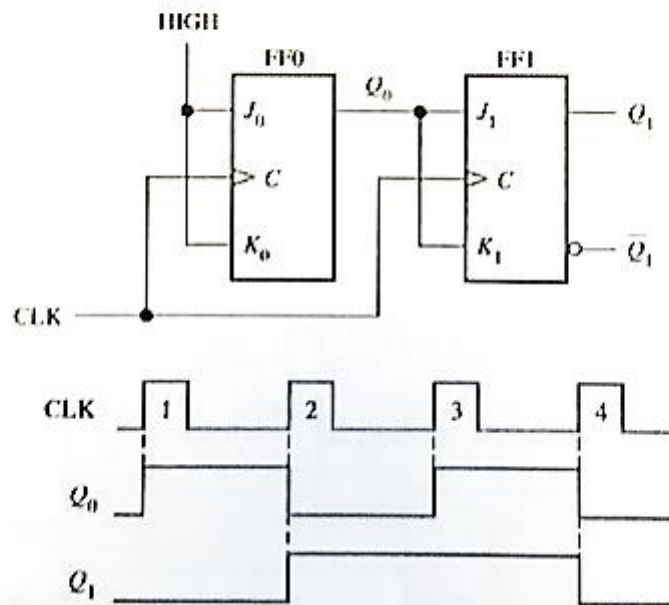

Synchronous counters

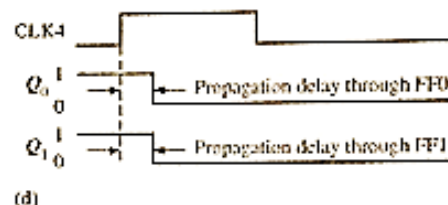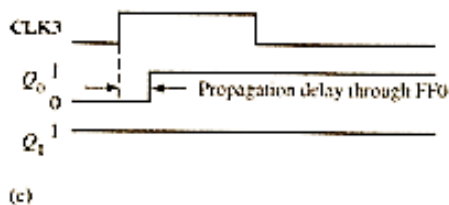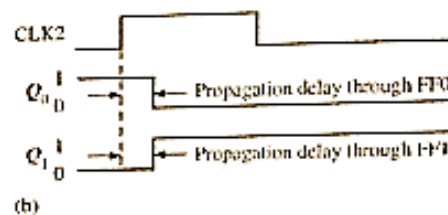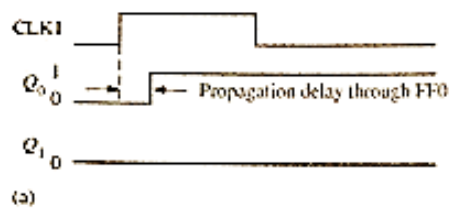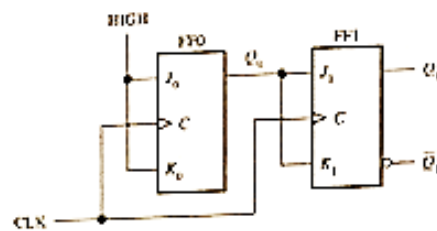Timing details for the 2-bit synchronous counter operation (the propagation delays of both flip-flops are assumed to be equal).



Synchronous counters

A 3-bit synchronous binary counter

